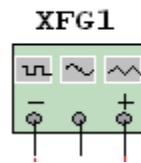


Lab Project 1


2Bit Binary Counter Simulation Notes

To simulate a 2Bit Binary Counter in Multisim requires two important pieces of test equipment: Function Generator and a Logic Analyzer

Function Generator



Logic Analyzer


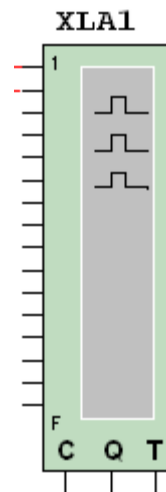


Lab Project 1

2Bit Binary Counter Simulation Notes

A Logic Analyzer is used for fast data acquisition of logic states and advanced timing analysis to help design large digital systems and carry out troubleshooting.


Logic Analyzer

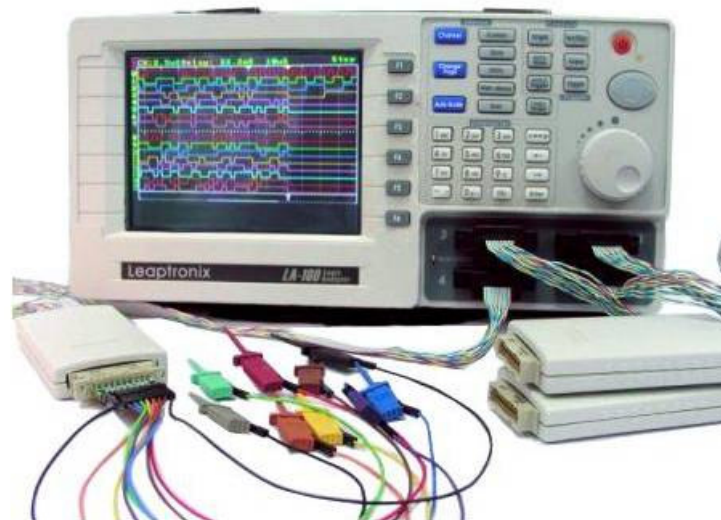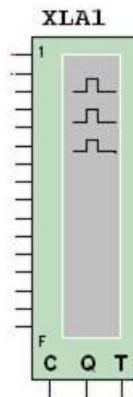

Lab Project 1

2Bit Binary Counter Simulation Notes

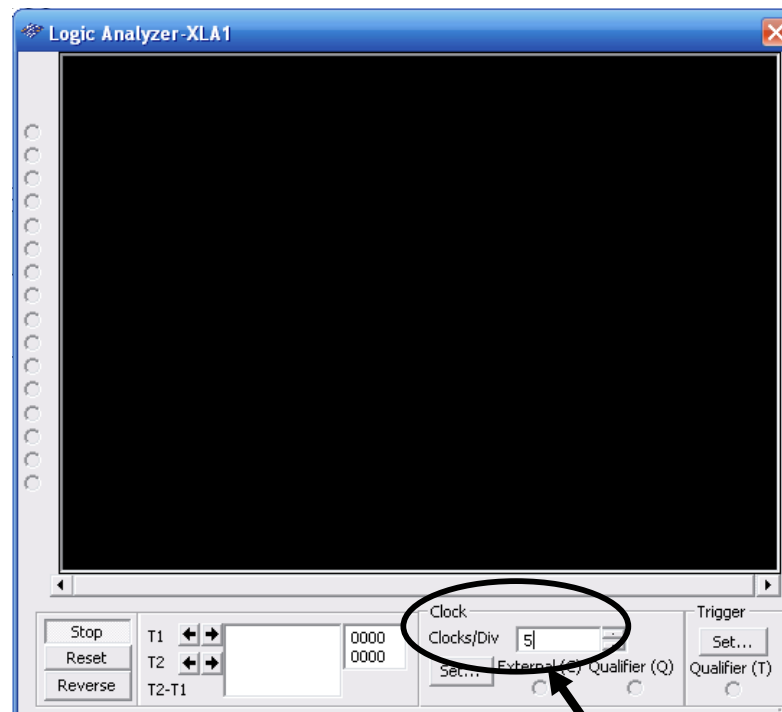Double click the Logic Analyzer Icon with the mouse and adjust the test instrument as shown in the Figure below.




Adjust Clocks/Div
to 5

Lab Project 1

2Bit Binary Counter Simulation Notes

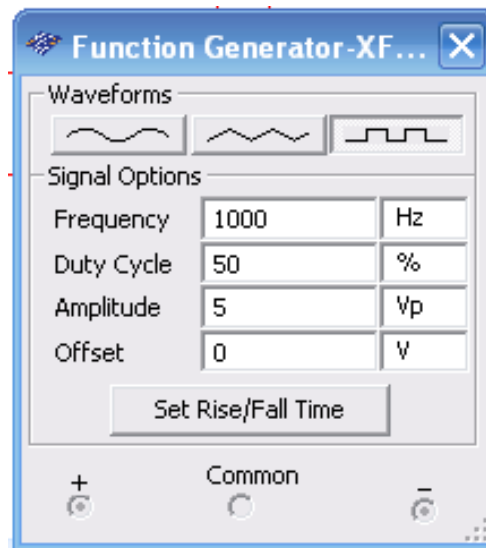Double click the Function Generator Icon with the mouse and adjust the test instrument as shown in the Figure below.





Lab Project 1


2Bit Binary Counter Simulation Notes

Lab Procedure

- Build the 2Bit Binary Counter in Multisim.
- Run a simulation event on the digital circuit.
- The Logic Analyzer shall display a series of square-wave pulses on the screen.

Lab Project 1


2Bit Binary Counter Simulation Notes

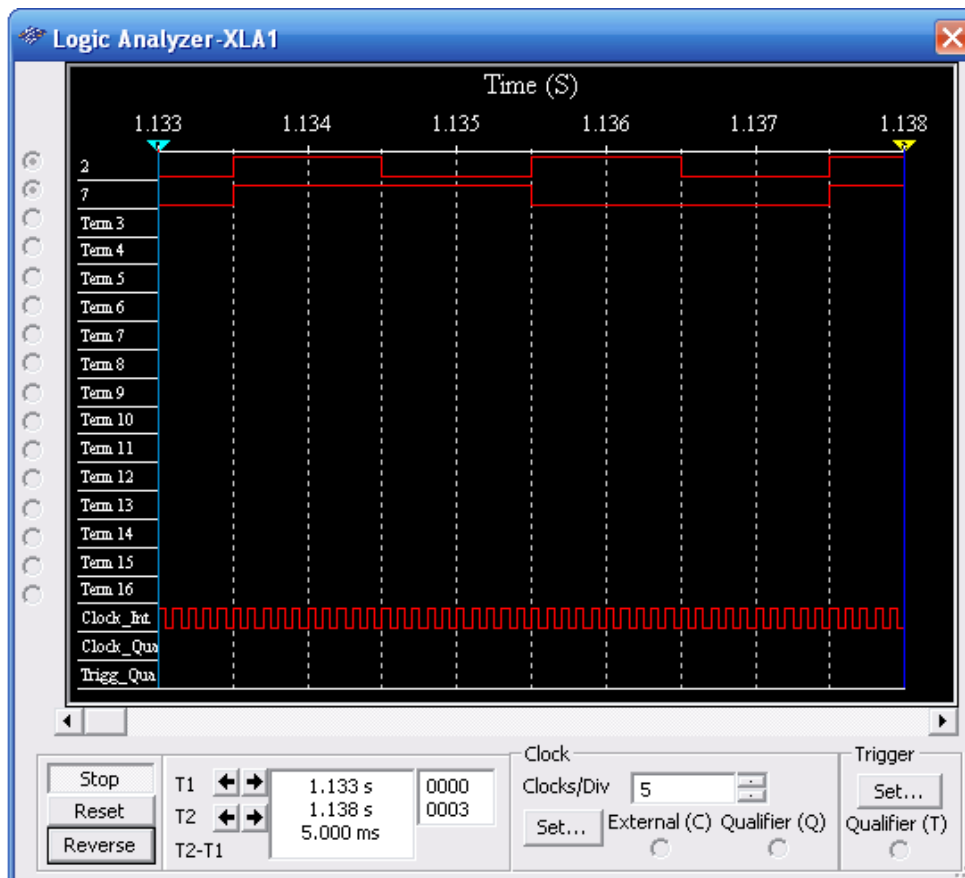

Lab Project 6

An Inverting Comparator

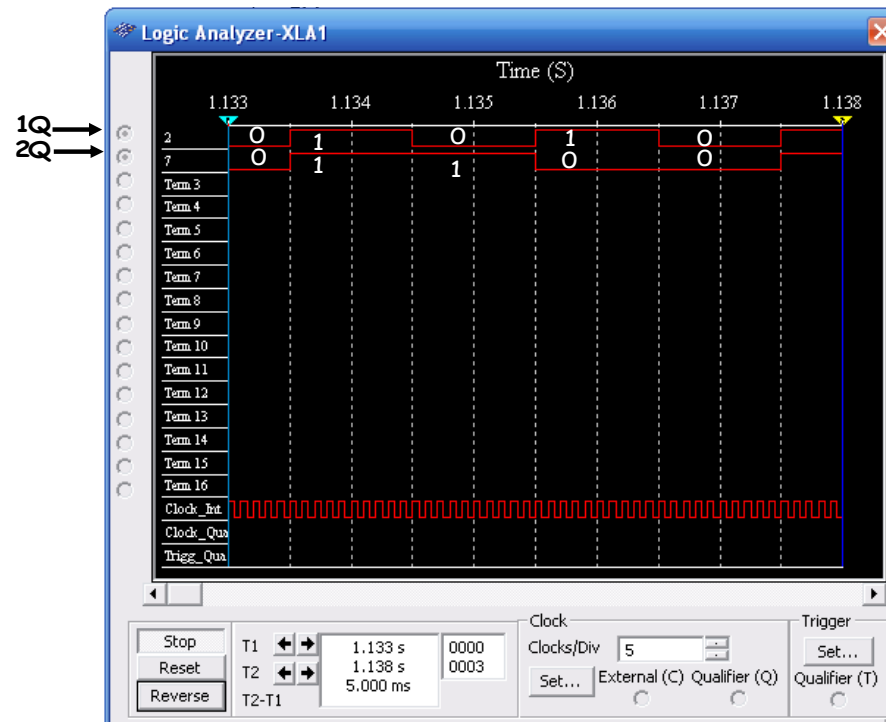Convert the square-wave pulses into Binary "1s" and "0s" data.



Lab Project 1

2Bit Binary Counter Simulation Notes

The Binary to Decimal Conversion Table shows the Count Value of the digital circuit.

2Q	1Q	Count Value
1	1	3
1	0	2
0	1	1
0	0	0